



Federal Board SSC Practical Examination
Name of subject **Internet of Things**
Hardware Development
Model Question Paper

Time Allowed: _____

Total Marks: 90

Written Examination (10)

- Q.1 What are the main pin sections on the Arduino board? (5)
OR
What is full wave rectifier? Explain with diagram.
- Q.2 Discuss how to create a powerful Gig. (5)
OR
How we can use Arduino as Wi-Fi Hotspot?

Practical Exam (60)

- Q.3 Design combinational circuit and verify using KVL. (15)
OR
Apply Ohm's Law for measuring current, voltage and resistance.
- Q.4 Construct a combinational circuit and measure current, voltage and resistance. (15)
- Q.5 Detect motion using ultrasonic sensor. (15)
OR
Turn on/off a light bulb connected with relay.
- Q.6 Verify the Truth Table of NAND Gate using NAND Gate IC. (15)

Viva Voce (20)